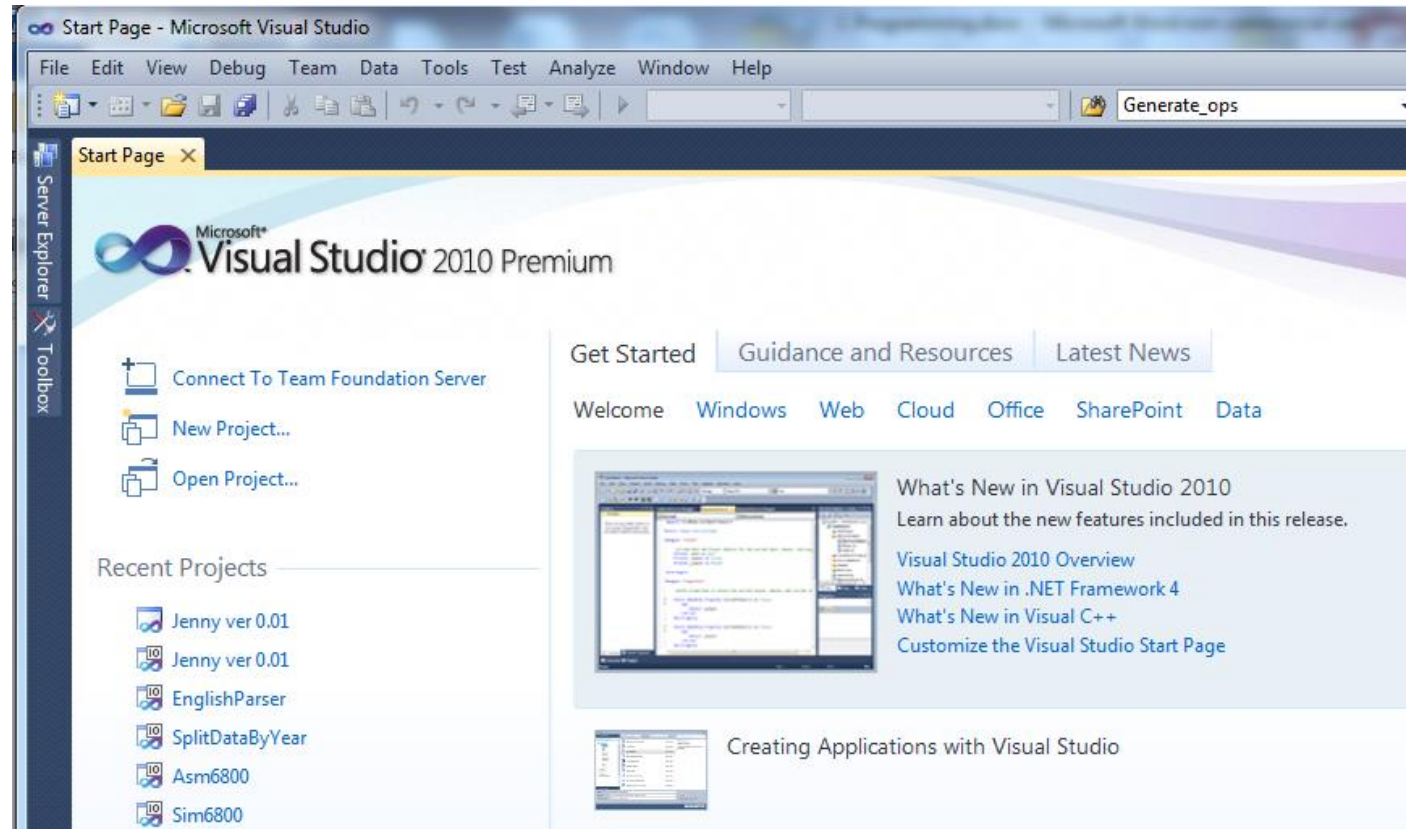


UFCF93-30-1 Computer and Network Systems


Computer Practical 4 Learning C
programming

C Programming




C Programming

1) Select New Project...

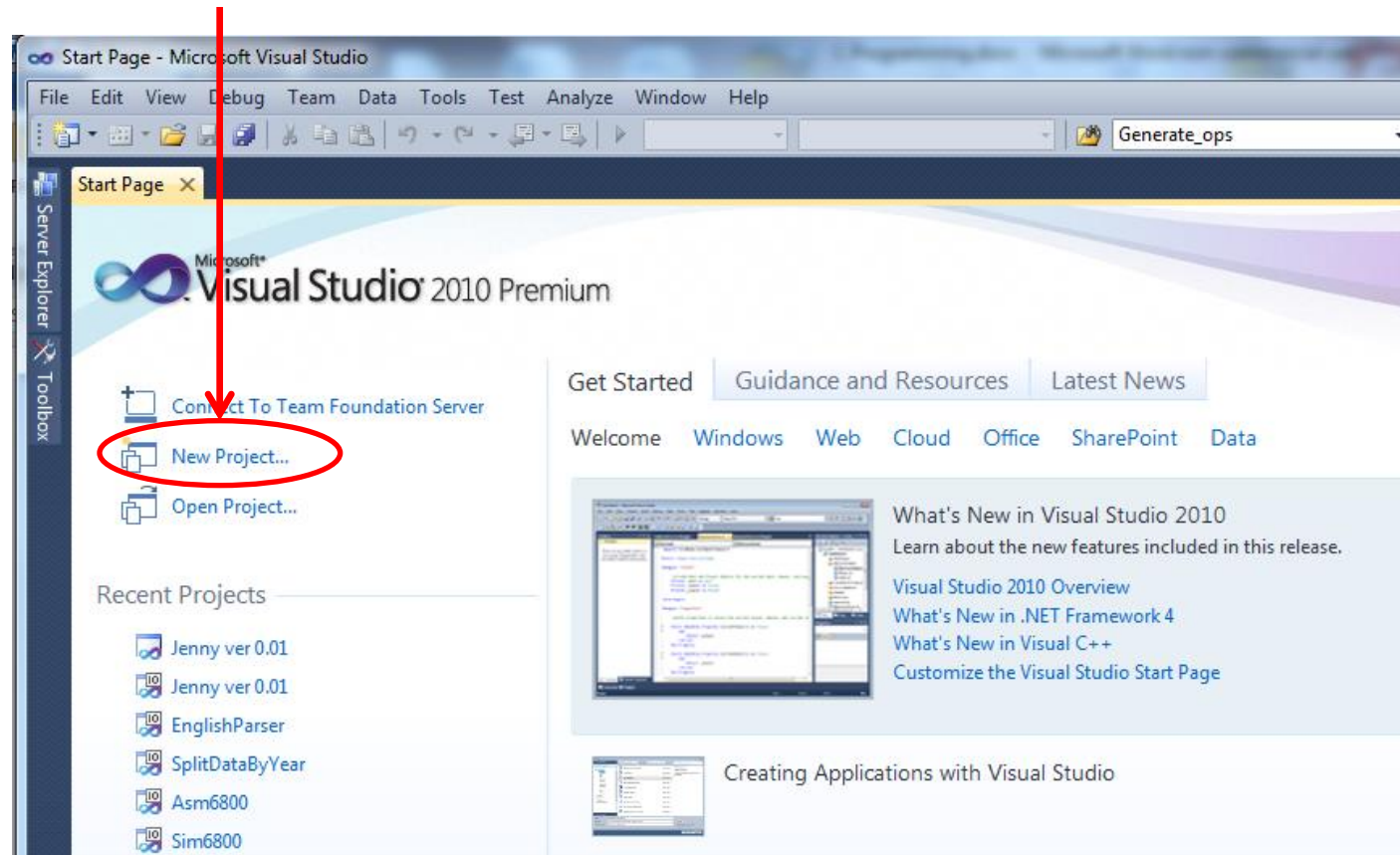


C Programming

1) Select Visual C++

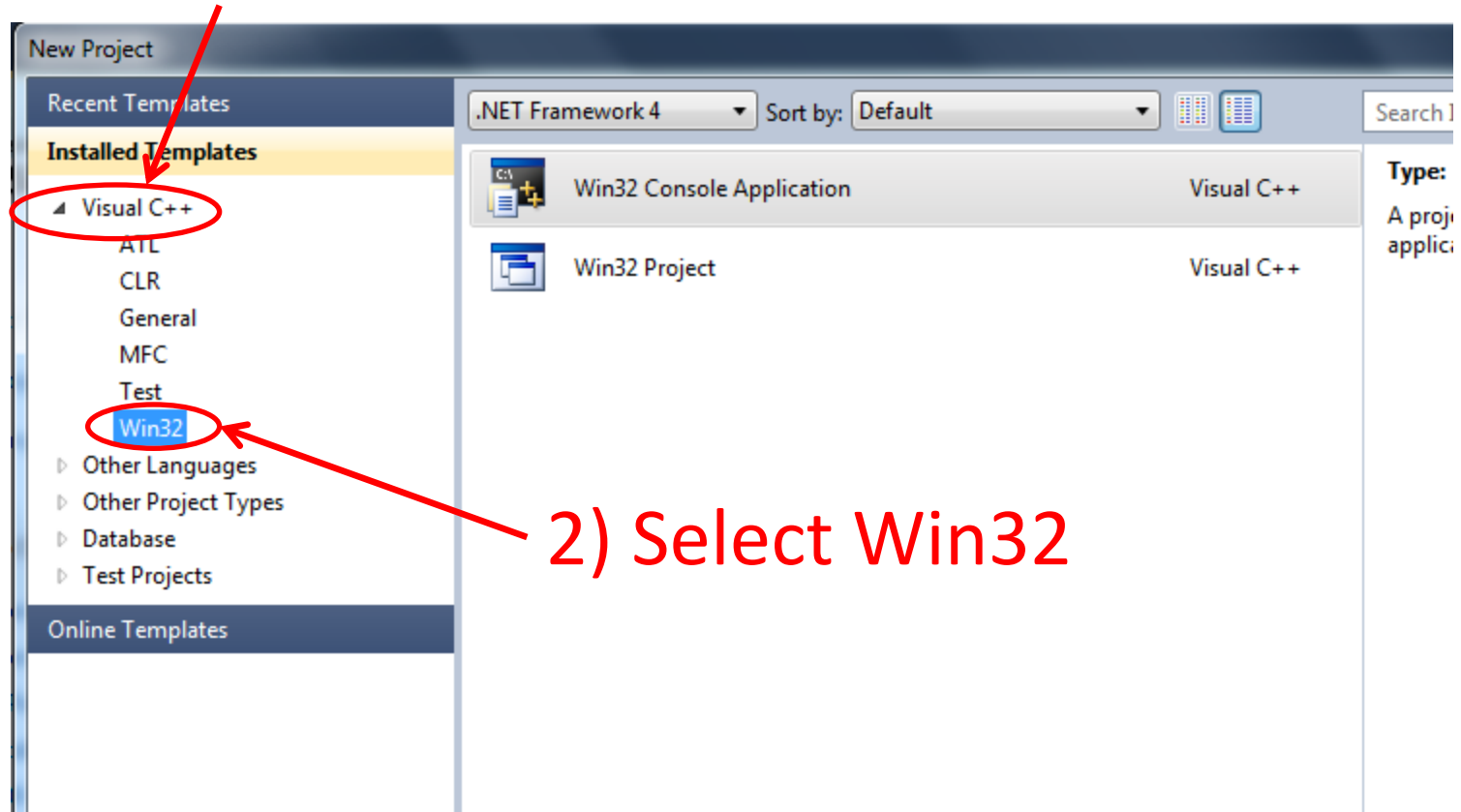


C Programming

1) Select Win32 Console Application

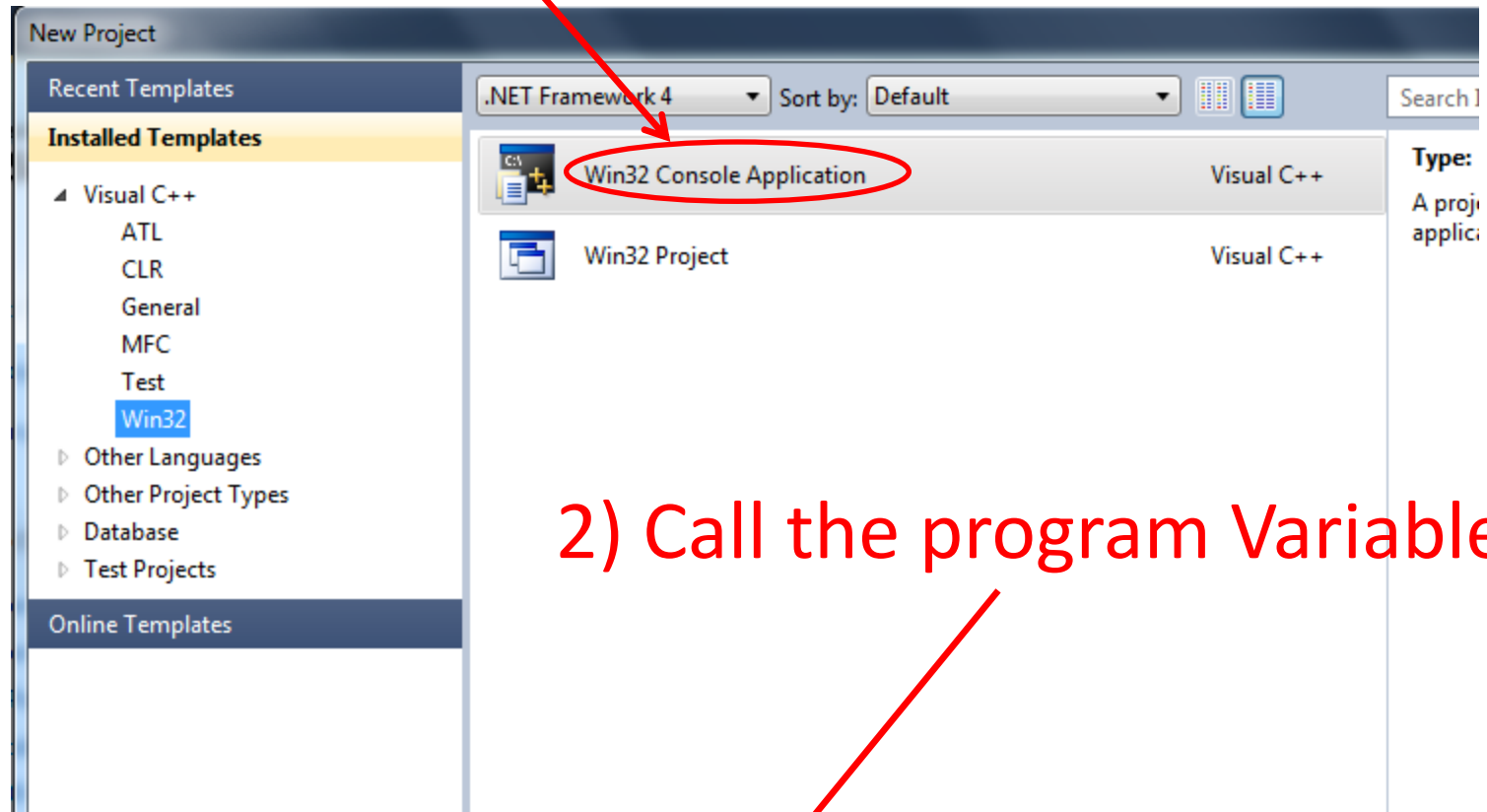


2) Call the program Variables


C Programming

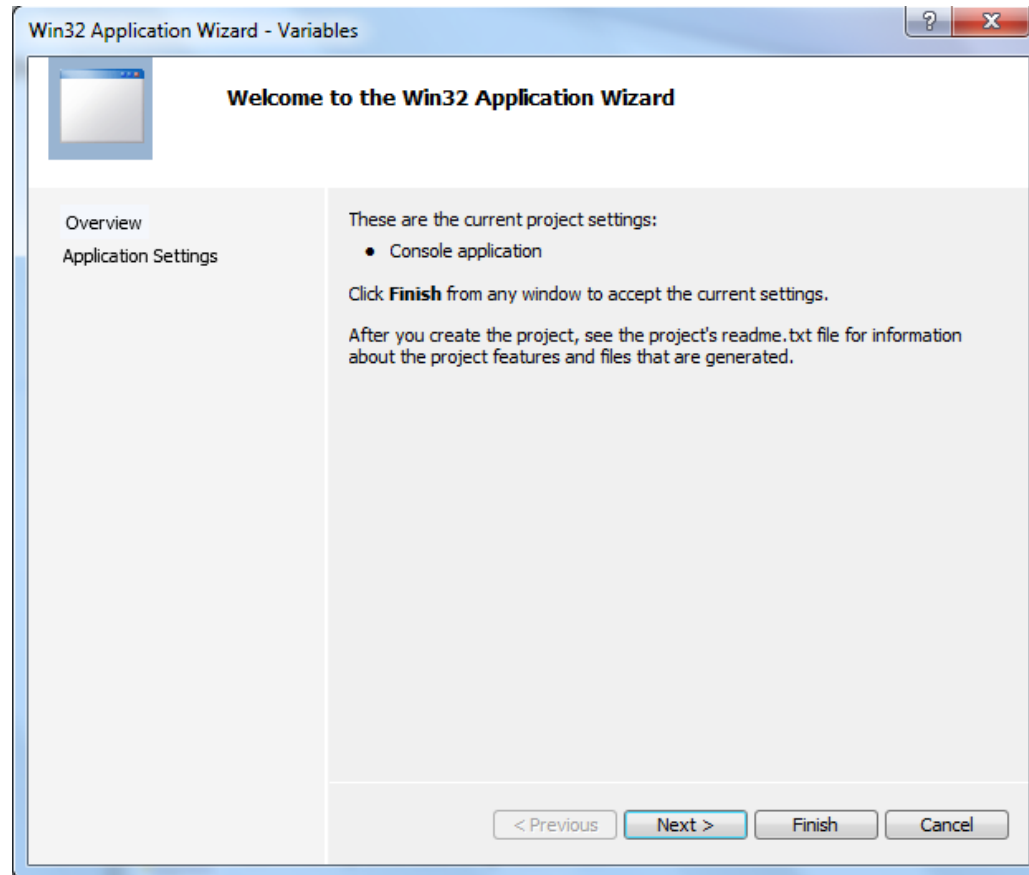

C Programming

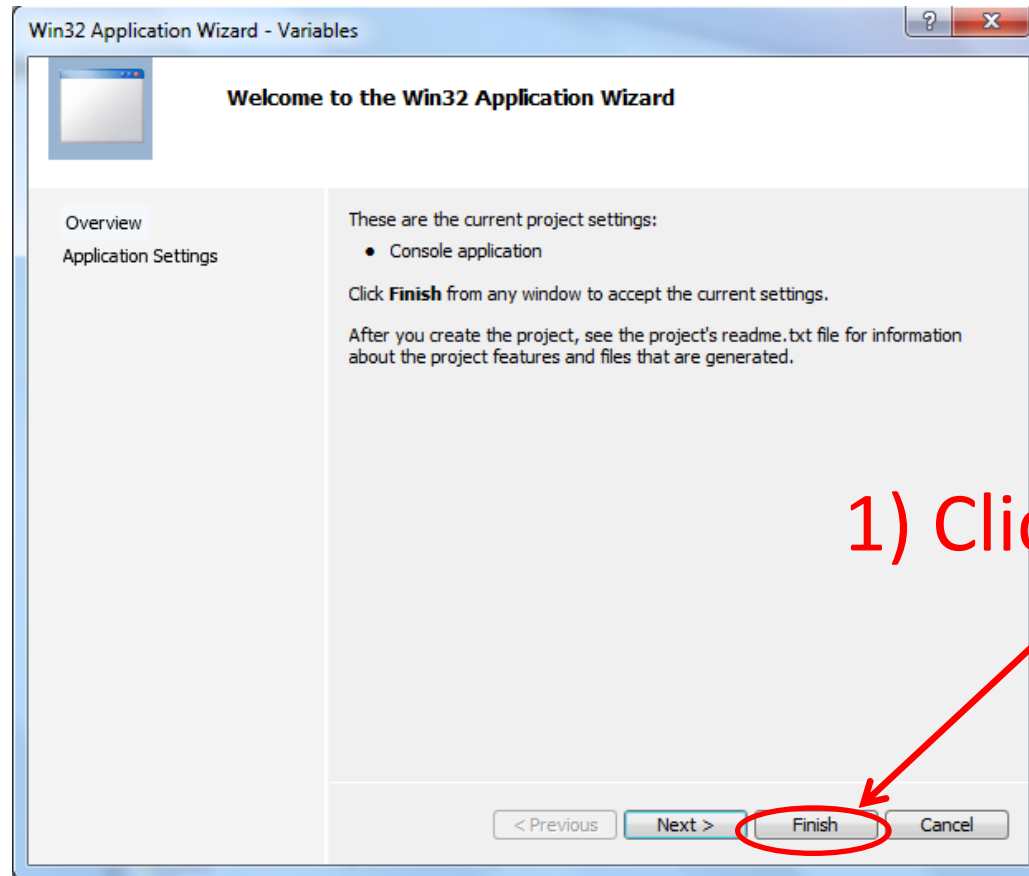


C Programming

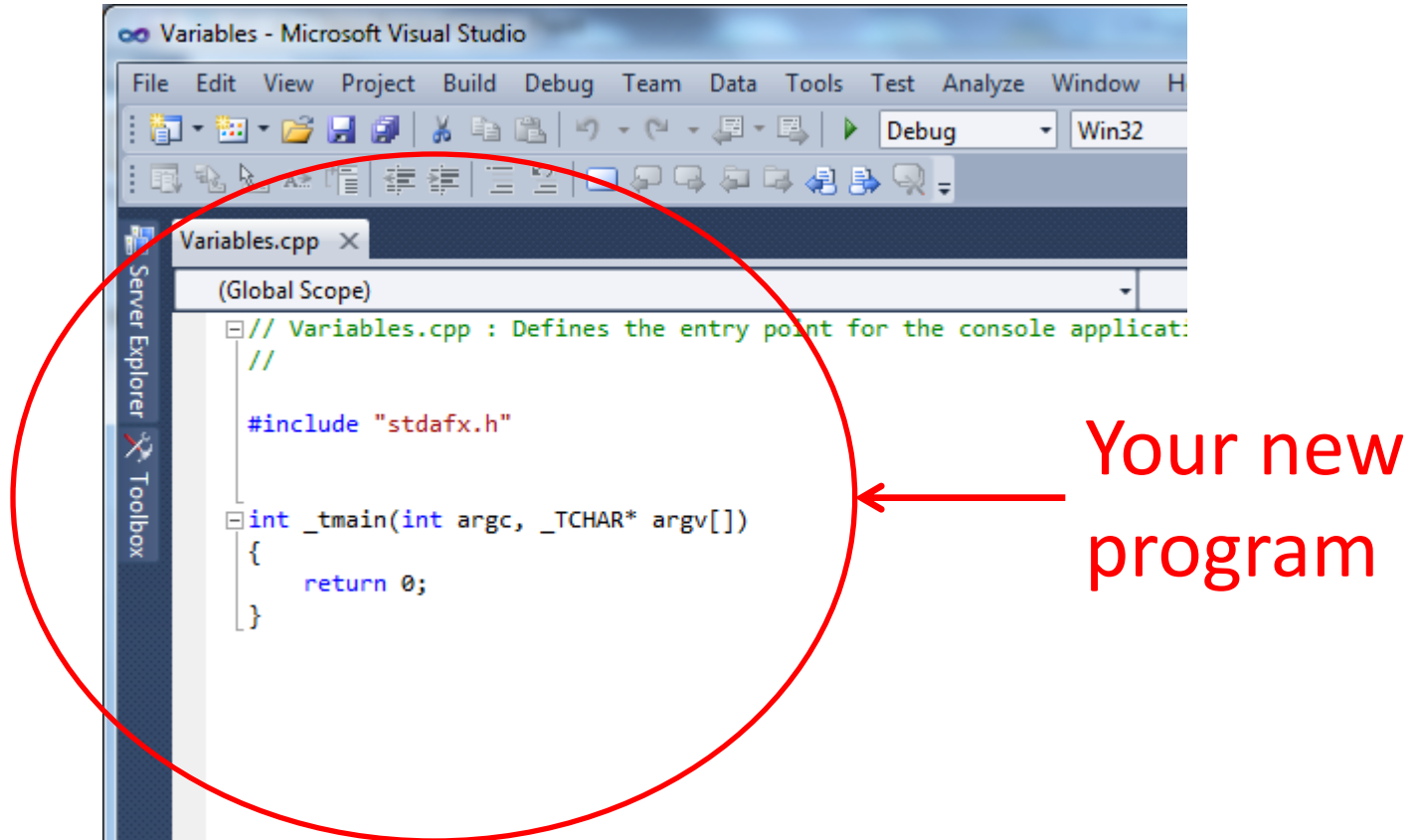

C Programming

2) Click Build

3) Click the green arrow

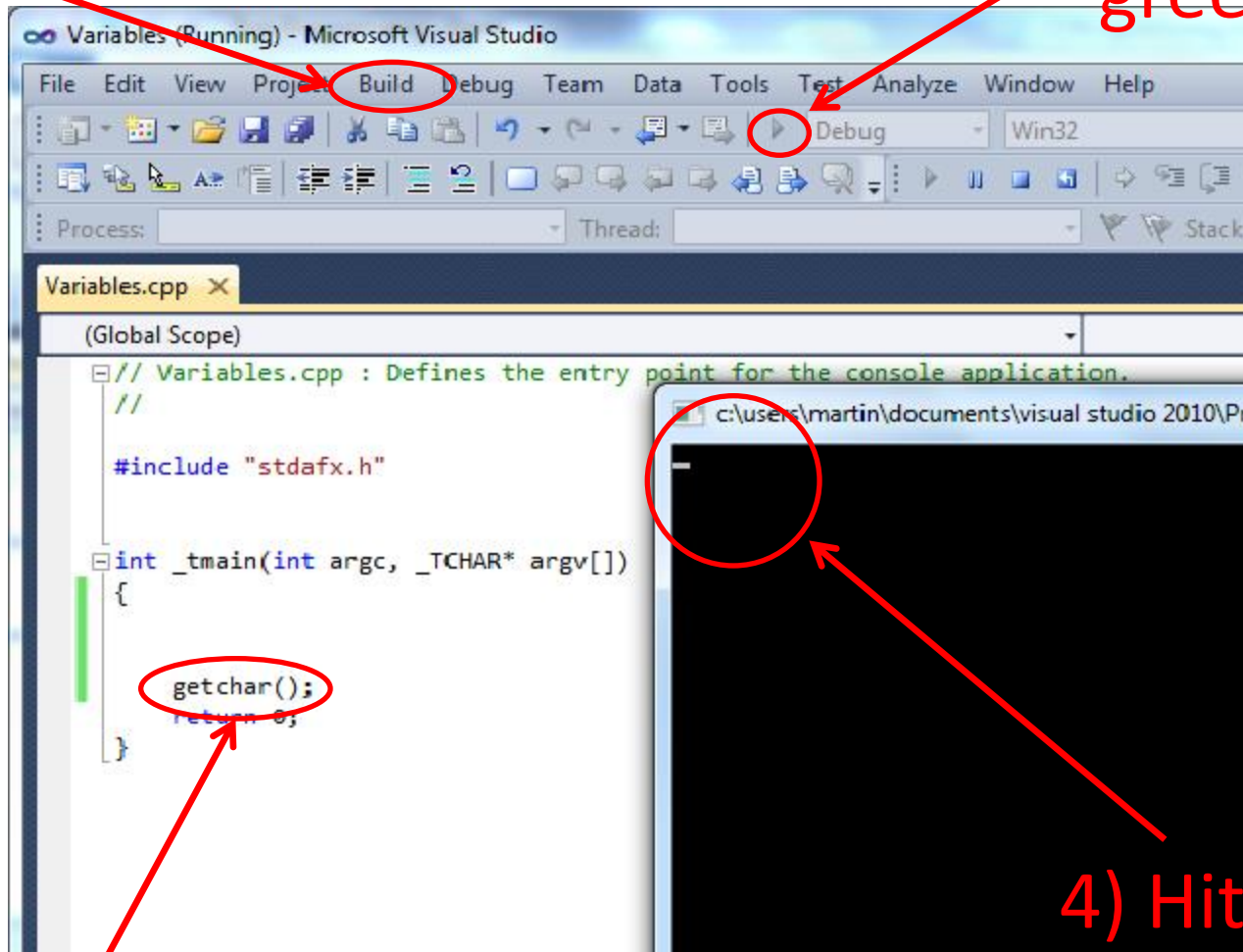


1) Add getchar();

4) Hit any key
to close the
program

C Programming – Adding Circuits

Half Adder Circuits add two single bit inputs together giving a sum and a carry

Looks like this...

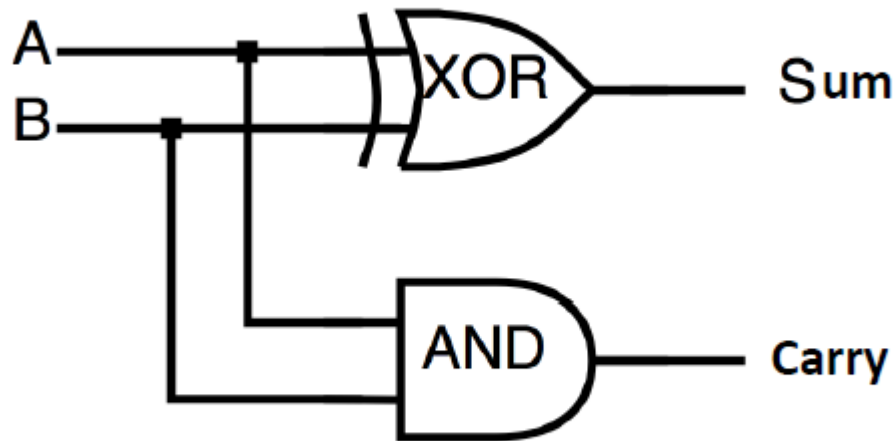


...and is called a half adder


C Programming – Adding Circuits

Half Adder Circuits add two single bit inputs together giving a sum and a carry

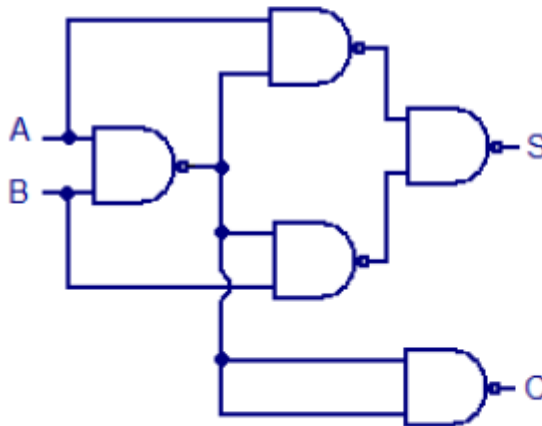Which can be re-written like this to remove the XOR...




Half adder using NAND logic

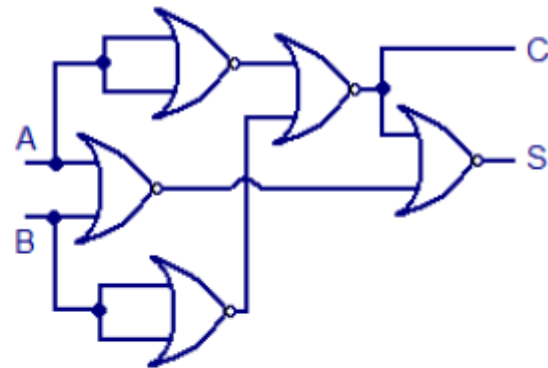

Half adder using NOR logic

C Programming – Adding Circuits

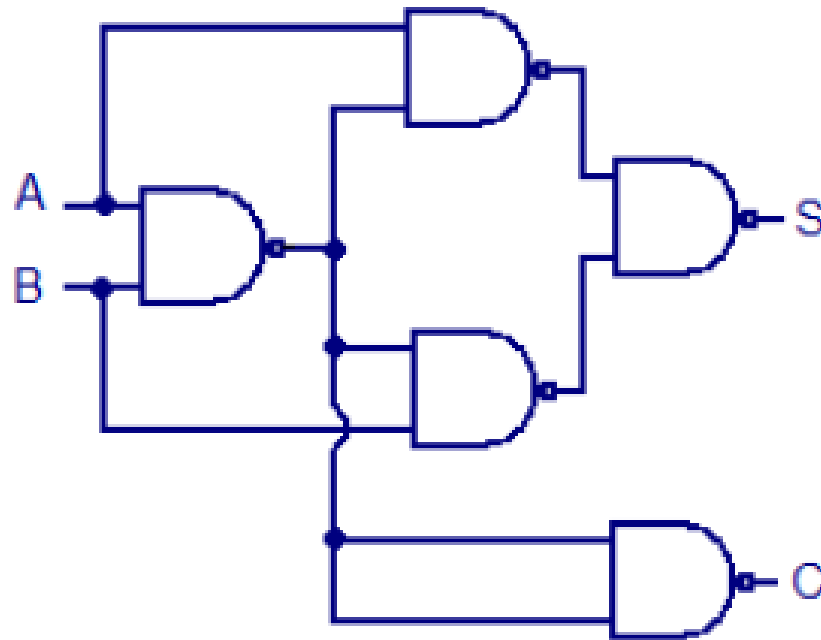
Lets create a C program to emulate a NAND gate half-adder circuit...



Half adder using NAND logic

C Programming – Adding Circuits

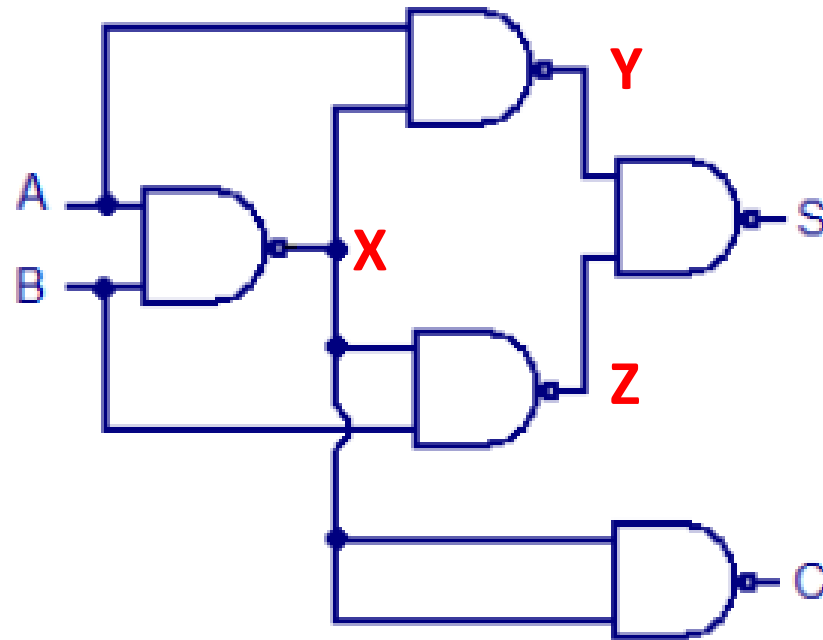Lets create a C program to emulate a NAND gate half-adder circuit...



Lets create some local variables X, Y and Z to make our life easier

Half adder using NAND logic

C Programming – Adding Circuits

Now lets write some C code, add a function to do a NAND above main()...

```
bool nand(bool input1, bool input2)
{
    return !(input1 && input2);
}
```

C Programming – Adding Circuits

This function returns a
boolean value

There are two boolean inputs

```
bool nand(bool input1, bool input2)
{
    return !(input1 && input2);
}
```

'return' returns a value of the same type as its
function (boolean in this case)

C Programming – Adding Circuits

Add the print() function from last week...

```
void print(char* name, bool d)
{
    if (d)
    {
        printf_s("%s = true\n", name);
    }
    else
    {
        printf_s("%s = false\n", name);
    }
}
```


C Programming – Adding Circuits

Update main()...

```
int _tmain(int argc, _TCHAR* argv[])
{
    bool a, b;
    bool x, y, z;
    bool sum;
    bool carry;


    a = false;
    b = false;

    x = nand(a, b);
    y = nand(a, x);
    z = nand(x, b);

    sum  = nand(y, z);
    carry = nand(x, x);

    print ("sum  ", sum);
    print ("carry", carry);

    getchar();
    return 0;
}
```

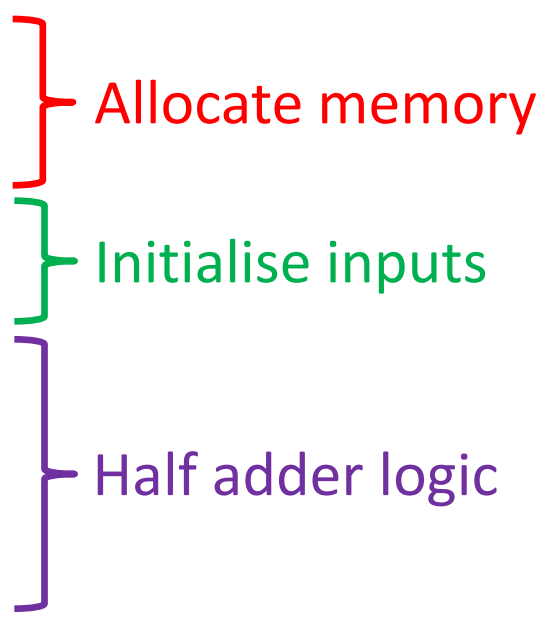

Allocate memory

Initialise inputs

Half adder logic

C Programming – Adding Circuits

Build and run...

```
int _tmain(int argc, _TCHAR* argv[])
{
    bool a, b;
    bool x, y, z;
    bool sum;
    bool carry;


    a = false;
    b = false;

    x = nand(a, b);
    y = nand(a, x);
    z = nand(x, b);

    sum  = nand(y, z);
    carry = nand(x, x);

    print ("sum  ", sum);
    print ("carry", carry);

    getchar();
    return 0;
}
```

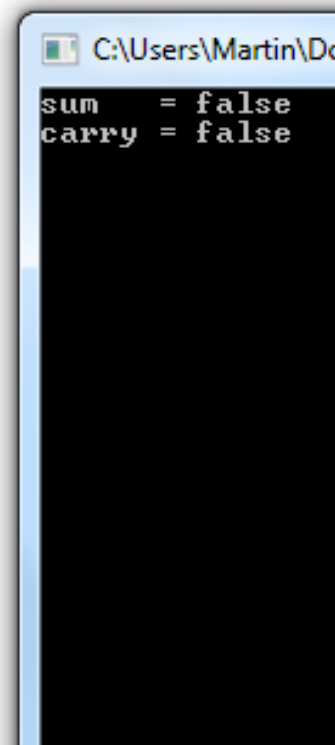A screenshot of a Windows command prompt window. The title bar shows the path 'C:\Users\Martin\Do...'. The window has a black background with white text. It displays the output of the C program: 'sum = false' and 'carry = false' on two separate lines.

```
C:\Users\Martin\Do...
sum  = false
carry = false
```

$a + b = \text{sum}, \text{carry}$

As false is 0 and true is 1
then $0 + 0 = 0$ carry 0

C Programming – Adding Circuits

Modify the program to complete the following table...

A	B	Sum	Carry
False	False	?	?
False	True	?	?
True	False	?	?
True	True	?	?


C Programming – Adding Circuits

Converting to zeroes and ones...

A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

C Programming – Adding Circuits

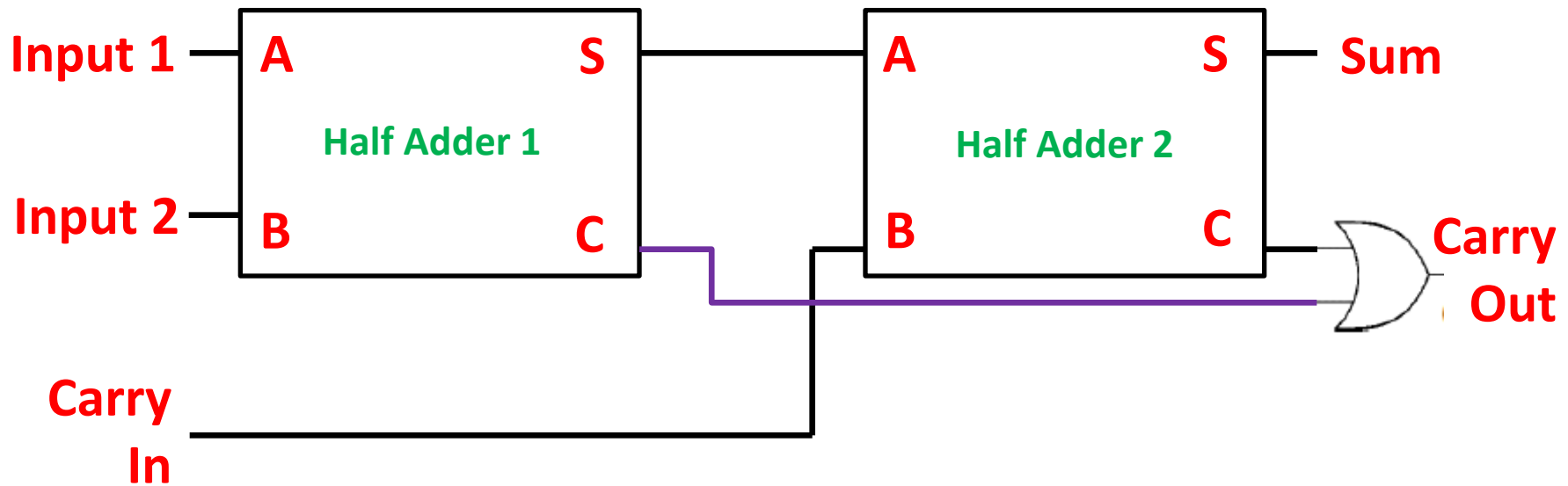Full Adder Circuits add two single bit inputs and an input carry together giving a sum and an output carry



C Programming – Adding Circuits

Lets emulate a full adder in C code, first lets create a half adder circuit...

It is a little harder as we want two inputs and two outputs...

```
void half_adder(bool input1, bool input2, bool* sum, bool* carry)
{
}
```

Inputs (by value)




Outputs (by reference)



C Programming – Adding Circuits
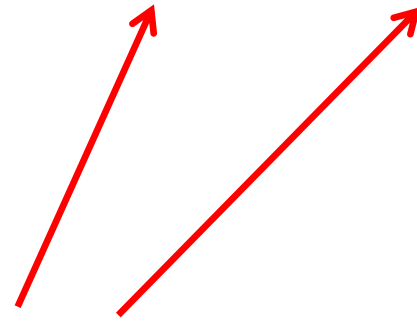
```
void half_adder(bool input1, bool input2, bool* sum, bool* carry)
{
}
```



The address of the variables, sum and carry, will be passed to this function so that the function can write updated values to them (Note that sum and carry are **pointers**)

C Programming – Adding Circuits

Let's finish off the half adder...

```
void half_adder(bool input1, bool input2, bool* sum, bool* carry)
{
```

`bool x, y, z;`

← Local variables

```
    x = nand(input1, input2);
```

```
    y = nand(input1, x);
```

```
    z = nand(x, input2);
```

```
    *sum = nand(y, z);
```

```
    *carry = nand(x, x);
```

} Half adder logic

↑
Write to what these pointers point at (known as dereferencing)

C Programming – Adding Circuits

Let's update main()...

```
int _tmain(int argc, _TCHAR* argv[])
{
    bool input1, input2, carry_in;
    bool s1, c1, s2, c2;
    bool sum;
    bool carry_out;

    input1  = false;
    input2  = false;
    carry_in = false;

    half_adder(input1, input2, &s1, &c1);
    half_adder(s1,      carry_in, &s2, &c2);
    sum = s2;
    carry_out = c1 || c2;

    print ("sum  ", sum);
    print ("carry", carry_out);

    getchar();
    return 0;
}
```

} Full adder logic

C Programming – Adding Circuits

Modify the program to fill in this table...

Input 1	Input 2	Carry in	Sum	Carry out
False	False	False	?	?
False	False	True	?	?
False	True	False	?	?
False	True	True	?	?
True	False	False	?	?
True	False	True	?	?
True	True	False	?	?
True	True	True	?	?

C Programming – Adding Circuits

Let's make a full adder function...

```
void full_adder(bool input1, bool input2, bool carry_in, bool* sum, bool* carry_out)
{
    bool s1, c1, s2, c2;

    half_adder(input1, input2, &s1, &c1);
    half_adder(s1, carry_in, &s2, &c2);
    *sum = s2;
    *carry_out = c1 || c2;
}
```

C Programming – Adding Circuits

Let's update main()...

```
int _tmain(int argc, _TCHAR* argv[])
{
    bool input1, input2, carry_in;
    bool s1, c1, s2, c2;
    bool sum;
    bool carry_out;

    input1  = false;
    input2  = false;
    carry_in = false;

    full_adder(input1, input2, carry_in, &sum, &carry_out);

    print ("sum  ", sum);
    print ("carry", carry_out);

    getchar();
    return 0;
}
```

C Programming – Adding Circuits

Modify the program to fill in this table...

Input 1	Input 2	Carry in	Sum	Carry out
False	False	False	?	?
False	False	True	?	?
False	True	False	?	?
False	True	True	?	?
True	False	False	?	?
True	False	True	?	?
True	True	False	?	?
True	True	True	?	?

...is it the same as before?

C Programming – Adding Circuits

Let's do some 4-bit maths...

```
int _tmain(int argc, _TCHAR* argv[])
{
    bool input1[4] = {false, false, false, false};
    bool input2[4] = {false, false, false, false};
    bool carry_in = false;
    bool carry_temp;
    bool sum[4];
    bool carry_out;

    full_adder(input1[0], input2[0], carry_in, &sum[0], &carry_temp);
    full_adder(input1[1], input2[1], carry_temp, &sum[1], &carry_temp);
    full_adder(input1[2], input2[2], carry_temp, &sum[2], &carry_temp);
    full_adder(input1[3], input2[3], carry_temp, &sum[3], &carry_out );

    print ("sum[0]  ", sum[0]);
    print ("sum[1]  ", sum[1]);
    print ("sum[2]  ", sum[2]);
    print ("sum[3]  ", sum[3]);

    print ("carry   ", carry_out);

    getchar();
    return 0;
}
```

C Programming – Adding Circuits

```
int _tmain(int argc, _TCHAR* argv[])
{
    bool input1[4] = {false, false, false, false};
    bool input2[4] = {false, false, false, false};
    bool carry_in = false;
    bool carry_temp;
    bool sum[4];
    bool carry_out;

    full_adder(input1[0], input2[0], carry_in, &sum[0], &carry_temp);
    full_adder(input1[1], input2[1], carry_temp, &sum[1], &carry_temp);
    full_adder(input1[2], input2[2], carry_temp, &sum[2], &carry_temp);
    full_adder(input1[3], input2[3], carry_temp, &sum[3], &carry_out );

    print ("sum[0] ", sum[0]);
    print ("sum[1] ", sum[1]);
    print ("sum[2] ", sum[2]);
    print ("sum[3] ", sum[3]);

    print ("carry ", carry_out);

    getchar();
    return 0;
}
```

Initialises input1[0]

Initialises input1[3]

Inputs

Temporary variable

Outputs

C Programming – Adding Circuits

Remember that the 4-bit inputs are initialised in the order of bit 0 to 3

So, to set input1 to 1010 in binary we write...

```
bool input1[4] = {false, true, false, true};
```

1 0 1 0



C Programming – Adding Circuits

Modify the program to fill in this table...

Input 1	Input 2	Carry in	Sum	Carry out
1010	0000	0	?	?
1010	0101	0	?	?
1010	0101	1	?	?
1111	0000	0	?	?
1111	0000	1	?	?
1111	1111	0	?	?
1111	1111	1	?	?
1011	0111	0	?	?

C Programming – Adding Circuits

Hopefully you can see how simple **NAND** and **NOR** gates can be used to do **integer addition**

The End